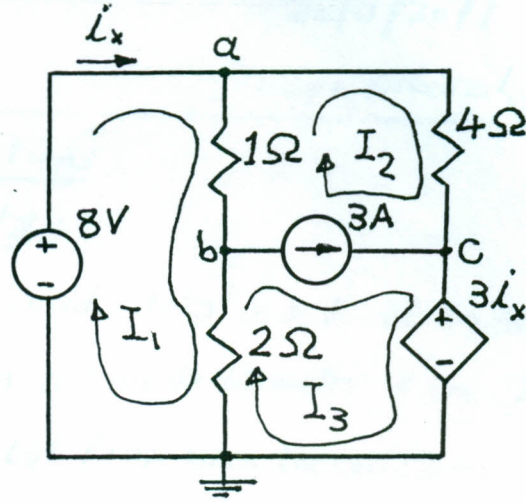


تصريحه دوانسره لهر بيه
 اولي لهر بيار
 "صحيح"
 ۴. د حال سبيل ورغه ذوو به واحد
 ۴. د محمد عادل راتبه بس ورغه ذو و جرين

Mansoura University	Electric Circuits (1)
Faculty of Engineering	1 st Year Elec. Power Dept.
December 2010	Time Allowed : 3 Hours


Please attempt all questions.

(1-a) Use Nodal-voltage analysis method to determine the current passing through the $2\text{-}\Omega$ resistor.




(1-b) Use Mesh-current analysis method to determine the voltage across the 3A current source.

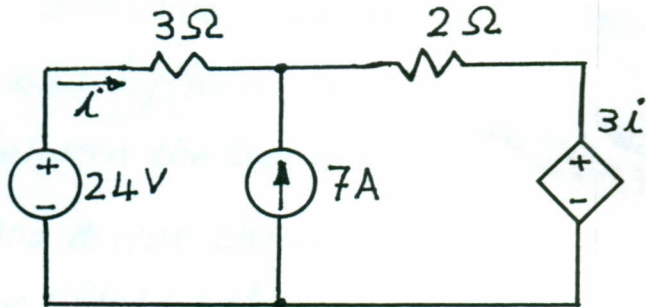(2-a) Using the superposition theorem for the shown circuit, determine the value of current "i".



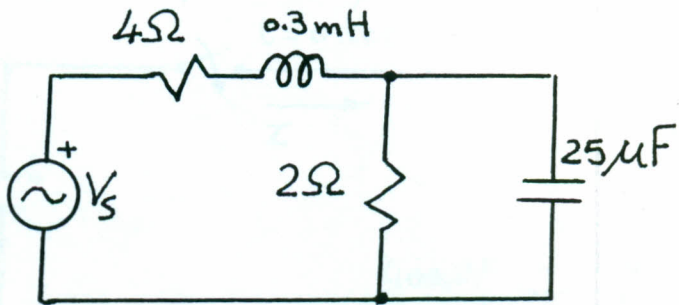(2-b) Determine the power delivered by the source for the shown circuit, given that the source voltage is 20 V and $\omega = 10,000\text{ rad/sec}$.



(3) The shown 3-ph, delta-connected load is supplied from a 3-ph, 130 V source;

Determine;

- The phase currents I_{AB} , I_{BC} , & I_{CA} .
- The line currents I_A , I_B , & I_C .

©The 3-ph consumed power.

