



Course: selected topic(5)
Fourth year

Jan. 2020
Time: 3-Hours

Answer all of the following questions

Question (1)

(20 Marks)

- 1- Sketch the on-grid solar energy system block diagram.
- 2- Explain how can you synchronize the output of the inverter with the grid voltage?
- 3- Design a pure sine wave inverter with the following specs:
 - a- 50 Hz
 - b- 220 Output voltage
 - c- 24 volt input voltage

Draw the corresponding circuit diagrams and the concerned signals.

Question (2)

(20 Marks)

- 1- Explain in details the modified 3 phase sine wave inverter, draw then the different signals and the corresponding arduino control circuit. Write then the corresponding code/flowchart.
- 2- Explain why we perform maximum power point tracking? Illustrate with curves
- 3- Explain in details the MPPT P&O algorithm.

Question (3)

(30 Marks)

Design A solar energy system for a villa situated at Luxor city. The villa contains 5 rooms , two bathrooms one kitchen and 2000 meter garden. The energy needed for the villa is given in the following table:

	Load	quantity	Power (watt)	Time / day In Hours	#Days / week
1	Internal lamps	10	100	5	7
2	Led TV 55 inches	2	200	7	7
3	Air conditions	4	2000	8	7
4	Air conditions	1	3000	6	7

The kitchen and the bathrooms are equipped with the following appliances :

	Load	quantity	Power (watt)	Time / day In Hours	#Days / week
1	Washing m/c	20	10	7	7
2	frigo	1	250	12	7
3	Air condition	1	2000	5	6
4	Water heater	1	1000	6	7
5	others		1000	2	5

The garden has the following loads:

	Load	quantity	Power (watt)	Time / day In Hours	#Days / week
1	Pump	1	3000	2	3
2	External lamps	10	50	6	7

The design should include the number and specs of each of the following:

- a) # Solar modules
- b) Charge controllers
- c) Inverters
- d) Batteries
- e) Array supports
- f) Transistor of the Inverter ratings

Good Luck