

Mansoura University	Electrical Eng. Dept.
Faculty of Engineering	1 st Year, January 2014
Time allowed : 3 Hours	Electric Circuits(1)


PART (A)

Please Answer all questions (Don't use pencil).

First Question : (8 Marks):


For the shown circuit,

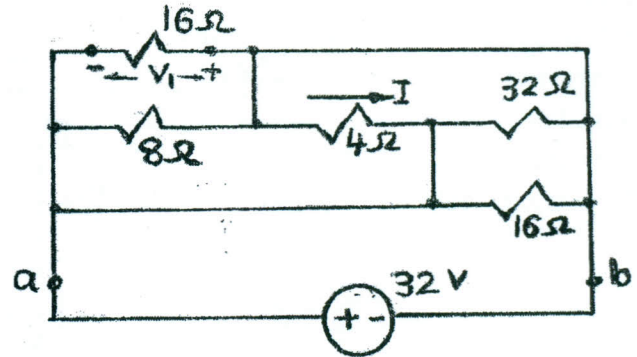- a-determine R_{ab} .
- b-calculate V_1 .
- c-determine the current I .



Second Question: (10 Marks):

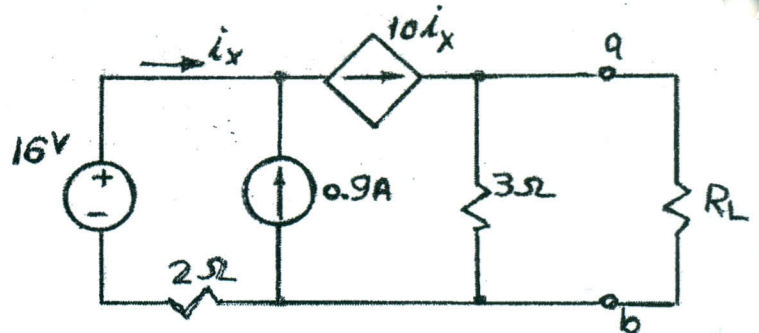
For the shown circuit, determine the value of resistor " R_L " that consumes maximum power. Determine this maximum power.



Third Question: (14 Marks):


For the shown circuit,

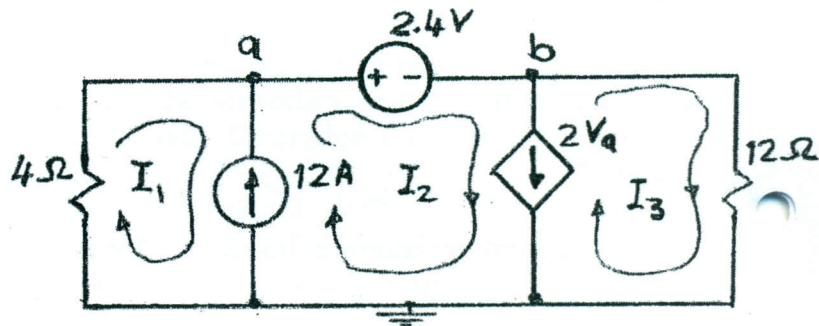- a-write the necessary nodal voltage method equations to determine V_a and V_b .(do not solve the equations).
- b- write the necessary mesh-current method equations to determine I_1 , I_2 , and I_3 .(do not solve the equations).



Fourth Question: (10 Marks):

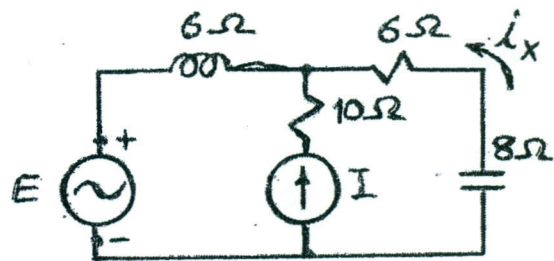Using the superposition theorem, determine the value of the current i_x for the shown circuit. Consider, $E_1 = 20 \angle 30^\circ$, and $I = 2\sqrt{2} \sin \omega t$.




Please turn over

Fifth Question: (8 Marks):

In a certain circuit, if $V_1 = 3\cos 4t$, and $V_2 = 4\sin(4t + 20^\circ)$, find the value of $(V_1 + V_2)$. Write the result in time-domain and in phase-domain forms.

Sixth Question: (10 Marks):

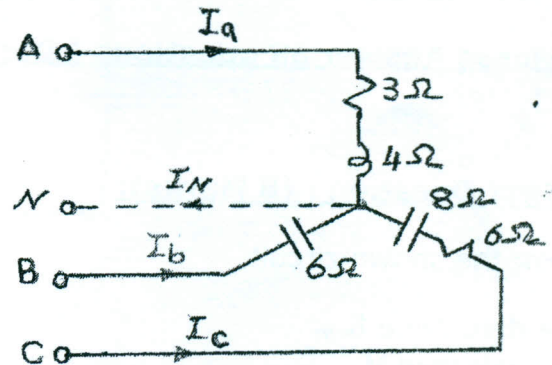A 3-ph supply with voltage of $V_s = 380 \sin 314t$ V, is supplying the 3-ph load shown in figure. Calculate;
a- The line currents I_a , I_b , and I_c .
b- The neutral current I_N .
c- The total power consumed by the load.




WITH MY BEST WISHES

Prof. Dr. Kamal Shebl

Part [2]

Frist Question:

- 1-a) Explain the origin of the fringing and leakage flux. (4 Marks)
 1-b) Sketch a typical hysteresis loop for a sample of ferromagnetic material and explain its shape, sketch also the typical hysteresis loop for; soft iron, hard steel, and Ferrite. (4 Marks)
 1-c) In the magnetic circuit shown in the following Figure, estimate the current, I.
 $\Phi = 100 \mu W$; $\mu_r = 1000$; $b = 3 \text{ cm}$; $l_1 = 20 \text{ cm}$; $l_2 = 8 \text{ cm}$; $t = 1 \text{ mm}$; $d = 2 \text{ cm}$. (12 Marks)

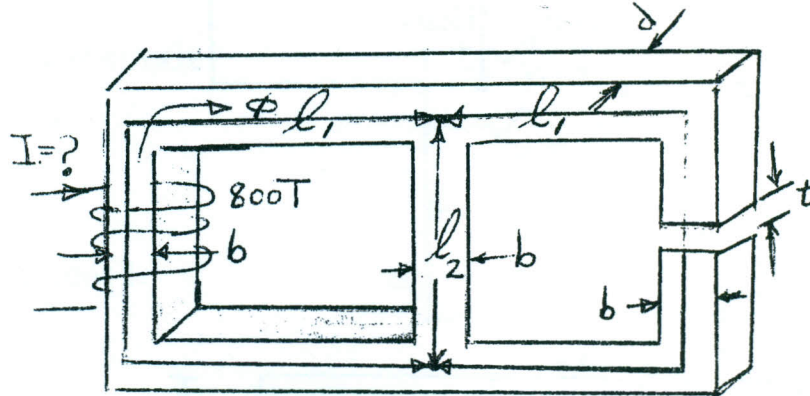

Second Question:

2-a) Prove, the self-inductance, $L = N \frac{\Delta\Phi}{\Delta i} = \frac{\mu_o \mu_r N^2 A}{l}$

Mutual inductance, $M = k N_p N_s \mu_o \mu_r \frac{A}{l} = K \sqrt{L_1 L_2}$

Stored energy in an inductive circuit, $W = \frac{B^2 A l}{2 \mu_o \mu_r}$ (6 Marks)


- 2-b) The dimensions of the magnetic core are; $A = 8 \text{ cm}$, $l = 20 \text{ cm}$, and relative permeability is 1000. The primary coil has $N = 1000$ turns, and the secondary coil has 600 turns. If the current is increased from zero to 8A in 0.3 seconds. Determine the emf induced in the secondary coil. (7 Marks)

- 2-c) A cast steel ring, has $A = 2 \text{ cm}$, and $l = 12 \text{ cm}$. A 400 – turn coil is wound on the ring. Determine the coil inductance when the current is 1A. (Assume $\mu_r = 1000$). (7 Marks)

Third Question:


- 3-a) Prove the following are in seconds; the charging time constant, τ_c - discharging time constant, τ_d - transient time constant in R-L DC circuit. (5 Marks)

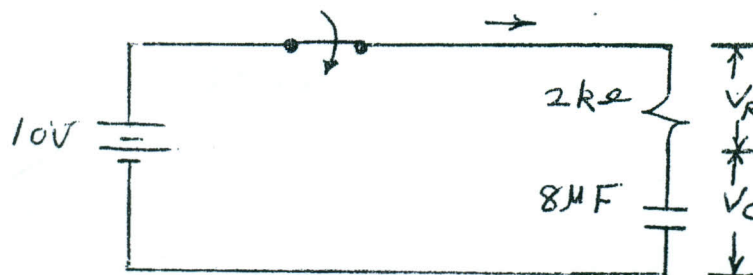- 3-b) (i) Calculate V_R and V_C at $t = \tau_c$, $t = 3\tau_c$, and $t = 5\tau_c$. (5 Marks)




(ii) Calculate V_C , and i_c at $t = \frac{1}{2}\tau_d$, $t = \tau_d$, and $t = 5\tau_d$. (Capacitor was fully charged at $t = 0$)

(5 Marks)

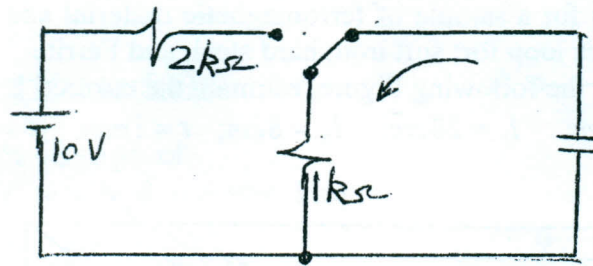

3-c) In the circuit shown, find;
 i_L , and V_L after τ , 3τ , and 5τ .

(5 Marks)

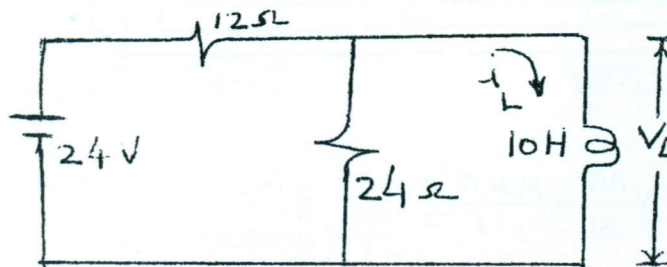

Good Luck. Prof. Adel El-Sayes