

Menoufia University Faculty of Engineering, Shebin El-Kom Mechanical Power Department First Semester Examination, 2013-2014 Date of Exam: Sunday 5/1/2014		Subject: Electrical Engineering Code: ELE117 Year: First Year MPD Time Allowed: 3 hours Total Marks: 60 marks
---	---	---

Answer the following questions, each has the same marks:

Question1: Six similar batteries, each has 24V and 0.6Ω internal resistance are connected as: 1- series, 2- parallel, 3- matrix (2X3) to a load resistance. For each case at maximum power transfer Find : the load resistance and the maximum power transfer.

Question2: An industrial process required lifting a 10 m^3 of hot water / minute at 85°C using a set of pump and electric motor. If the motor is fed from a 240 V dc supply at set efficiency is 85 % calculate: 1- the motor input power rating in Kw. 2- the motor current.

Question3: A simple series control circuit consists of two similar nonlinear resistors. If the battery voltage is 18 V and each nonlinear resistor has the following characteristics:

Volt(V)	0	2	4	6	8	9
Current(A)	0	0,1	0.2	0.5	0.9	1.5

For each resistor find: the current in, the voltage across and the power loss.

Question4: An iron ring has 2 m mean diameter, 20 Cm^2 cross-sectional area and 100000 relative permeability of the iron core. It wound uniformly with 1000 turns to produce 0.003 Wb in the core. Calculate:- the required current in the winding if the ring has:

- 1- no gap (i.e. $L_g = 0.0$), 2- a gap with $L_g = 2\text{Cm}$, $B_g = B_i$.

Question 5: A series R-L-C circuit operates at resonance. If $L=0.5\text{H}$, $C=10\mu\text{F}$ and $R=100\Omega$ calculate: 1- the supply frequency 2- the supply current. 3- the coil voltage. 4 - the input power. 5- the reactive power of the capacitor.

Question6: Resolve Question5 if C is parallel with (R-L) to find: the supply current and power at 50 Hz.

Question 7: The reading of the ammeter in Fig.1 is 8A. While the total current, $I = 15\text{A}$ with 45° leading angle. If the coil has $X_L = 10\Omega$, $r = 10\Omega$, calculate: 1- the supply voltage. 2- the unknown branch currents. 3- the values of R and C. 4- the equivalent impedance.

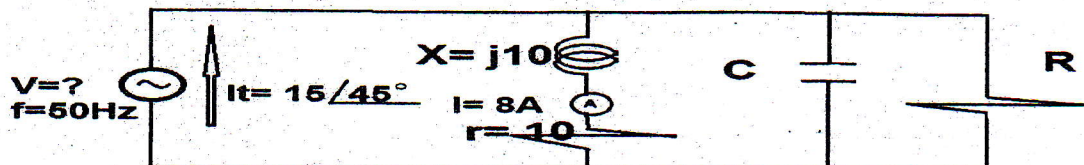


Fig. 1