



Answer The Following Questions

Question # 1 (15 Marks)

- A- Distinguish briefly between accuracy and precision. **(3 Marks)**
- B- Write expressions for R_x and L_x in the following Anderson AC bridge. Arm AB is the unknown inductance (R_x, L_x). Arm BC is a non-reactive resistance R_2 . DE is a resistance. Arm CD is a non-reactive resistance R_4 . Arm DA is a non-reactive resistance R_3 . EC is a capacitor C . EB is the detector and AC is the supply.
Then, calculate R_x and L_x if balance is obtained for $R_2=R_4=400 \Omega$, $R_3=500 \Omega$, $r=10 \Omega$, and $C=3\mu F$. **(3 Marks)**
- C- An electromagnetic wattmeter has voltage circuit resistance of 8000Ω and inductance of 63.6 mH which is connected directly across the load carrying 8 A at 50 Hz, voltage of 240 V and power factor of 0.1 lagging. Estimate percentage error in the wattmeter reading caused by the loading and inductance of the voltage coil. **(3 Marks)**
- D- Explain with the schematic diagram the speed measurement using photo-electric pickup tachometer. **(3 Marks)**
- E- A moving coil voltmeter has a uniform scale with 100 divisions and gives full-scale reading of 500 V. The instrument can read up to $1/10^{\text{th}}$ of a scale division with a fair degree of certainty. Determine the resolution of the instrument in volt. **(3 Marks)**

Question # 2 (15 Marks)

- A- Compare clearly between: **(6 Marks)**
(i) Direct and indirect methods of measurements.
(ii) Gross and systematic errors in measurements.
- B- Draw connection diagram for power measurement in a three-phase load using two-wattmeter method. **(2 Marks)**
- C- An ac bridge with terminals A, B, C, D (consecutively marked) has in arm AB a pure resistance; arm BC a resistance of 800Ω in parallel with a capacitor of $0.5 \mu F$; arm CD a resistance of 400Ω in series with a capacitor of $1.0 \mu F$; and arm DA a resistance of 1000Ω . Obtain the value of the frequency for which the bridge can be balanced. Also, calculate the value of the resistance in arm AB to produce balance. **(3 Marks)**
- D- Compare between the spring and gravity control methods. Use sketch diagrams as you can. **(4 Marks)**

Question # 3 (15 Marks)

- A- Explain with the aid of schematic diagram the elements of measurement system. (3 Marks)
- B- Show using sketches the constructional features of both types of moving iron instruments. (4 Marks)
- C- Explain the loading effect due to shunt and series connected instruments. (4 Marks)
- D- A shaded pole Induction ammeter is calibrated at 50 Hz. It gives a deflection of 105° with a current of 20 A. Determine the deflection of the instrument while measuring 20 A at a frequency of 75 Hz. (2 Marks)
- E- Schering bridge is used for measuring the loss angle of the capacitor. Explain this sentence. (2 Marks)

Question # 4 (15 Marks)

- A- State the merits and demerits of the following: (4 Marks)
(i) PMMC instruments (ii) Hot-wire instruments
- B- Compare between the recording and the integrating instruments. (2 Marks)
- C- State two methods which can be used for measurement of frequency? Explain the working of vibration reed frequency meter with its merits and demerits. (3 Marks)
- D- The inductance of a moving iron ammeter is $L = (10 + 5\theta - 2\theta^2) \mu\text{H}$ where θ is the angular deflection in radians from zero position. Determine the angular deflection in radians for a current of 10 A if the deflection for a current of 6 A is 40° . Also determine the spring constant. (3 Marks)
- E- Following readings were obtained in respect of measurement of a capacitor; 1.003, 0.998, 1.005, 0.996, 0.997, 1.008, and 0.994 nF. Calculate the arithmetic mean, the standard deviation, and the probable error of the mean value. (3 Marks)

With My Best Wishes
Associate Professor Dr. Ebrahim A. Badran