



Question (1)

(a) Write the missing numbers

i. $(257)_8 = (\dots)_2 = (\dots)_{16} = (\dots)_{10}$

ii. $(732)_{10} = (\dots)_5 = (\dots)_7 = (\dots)_9$

iii. $(A63)_{16} = (\dots)_{10} = (\dots)_8 = (\dots)_3$

b) i. List the digits from $(650)_7$ to $(1100)_7$

ii. List the digits from $(110)_3$ to $(1100)_3$

iii. Write the first 20 decimal digits in base 6

c) Subtract the following numbers using r's complement

i. $(38067)_9 - (58800)_9$

ii. $(549661)_{10} - (28700)_{10}$

[20 marks]

Question (2)

(a) implement the following function:

$F(X, Y, Z) = \Sigma(1, 3, 6, 7)$ using

I- NAND gates ONLY.

II- Multiplexer (8*1)

III-Decoder (3*8) + OR gate

IV- NOR gates ONLY.

V- Multiplexer (4*1)

(b) compare between full adder and full subtractor

[20 marks]

Question 3

a) Prove that full adder can be implemented by using two half adder and OR gate

b) Design a combinational circuit that accepts a three-bit number and generates an output binary number equal to the square of input number.

c) Design a BCD-to-excess-5 code converter, by using

1- Logic gates

2- MSI

d) Design a combinational circuit that has two inputs numbers each one with two bits. The output is determine by the following table

First number	Output
00	Second number + 3
01	Second number * 2
10	Second number * second number
11	Zero

- Obtain the truth table
- Find the simplified output function in sum of products.
- Find the simplified output function in product of sums.
- Implement the circuit by NAND gates ONLY.
- Implement the circuit by NOR gates ONLY.

[30 marks]

Question 4

a) Design a three-bit magnitude comparator

b) Design a five-bit binary adder

c) Design 8*1 multiplexer

d) Design 8*3 Encoder

e) Design 3*8 Decoder

[30 marks]

With all best wishes
Dr. Sabry F. Saraya