

- Question (1)** (a) Do the following subtraction using 8's complement after converting each number to base 9.  $(5432)_6 - (4240)_5 = (\dots\dots)_9$   
 (b) Write numbers between  $(90)_{12}$  to  $(110)_{12}$   
 (c) Using truth table to prove that  $(A \odot B \odot C \odot D) = (A \oplus B \oplus C \oplus D)'$   
 (d) Design a combinational circuit converts a decimal digits from the code (4 3 2 -1) to the code (6 3 -2 -1). Use the maximum number of (1's) in the representation of the input and output decimal digits (**hint:** don't implement the function) **[20 marks]**

**Question (2)** a) Implement full adder circuit by using only:

- i- Decoder (size 3\*8) and 2 OR gates.
- ii- 2 Decoder (size 2\*4) and 2 OR gates.
- iii- 2 Multiplexers (size 8\*1)
- iv- 2 Multiplexers (size 4\*1)

b) For the function  $F = A \oplus B \oplus C$  find:-

- 1. Truth table of F
- 2. F as Maxterms & Minterms
- 3. Implement F using NAND gates only
- 4. Implement F using NOR gates only

c) Prove that full-subtractor can be implemented with two half-subtractor + OR gate **[28 marks]**

**Question (3)** a) Design a combinational circuit that accepts a three-bit number and generates an output binary number equal to the square of input number.

b) Design a three-bit magnitude comparator

c) Design a five-bit binary adder/subtractor

d) Design a four bit binary parallel adder. **[22 marks]**

**Question (4)** a) Design an encoder to convert the decimal integer N to the binary integer  $(ABC)_2$ , as defined by the given table using OR gate only

N	A	B	C
0	0	0	0
1	0	0	1
2	0	1	1
3	0	1	0
4	1	1	0
5	1	0	0

b) Design a decoder to convert the binary integer  $(ABC)_2$  to decimal integer N, as define by the table in problem No (4-a)


c) Design a BCD adder.

d) Using ASCII table to write "Computer and System Department".

e) Analyze the two-output combinational circuits shown in fig. Obtain the Boolean functions for the two inputs and explain the circuit operation, then find  $(F_1 + F_2 + F_1'F_2')$  as a sum of minterms & product of maxterms **[30 marks]**

$B_7B_6B_5B_4$	$B_7B_6B_5$							
	000	001	010	011	100	101	110	111
0000	NULL	DLE	SP	0	@	P	.	p
0001	SOH	DC1	!	1	A	Q	a	q
0010	STX	DC2	"	2	B	R	b	r
0011	ETX	DC3	#	3	C	S	c	s
0100	EOT	DC4	\$	4	D	T	d	t
0101	ENQ	NAK	%	5	E	U	e	u
0110	ACK	SYN	&	6	F	V	f	v
0111	BEL	ETB	'	7	G	W	g	w
1000	BS	CAN	(	8	H	X	h	x
1001	HT	EM	)	9	I	Y	i	y
1010	LF	SUB	*	:	J	Z	j	z
1011	VT	ESC	+	:	K	[	k	{
1100	FF	FS	<	<	L	\	l	
1101	CR	GS	.	=	M	]	m	}
1110	SO	RS	.	>	N	^	n	~
1111	SI	US	/	?	O	_	o	DEL

ASCII Code table

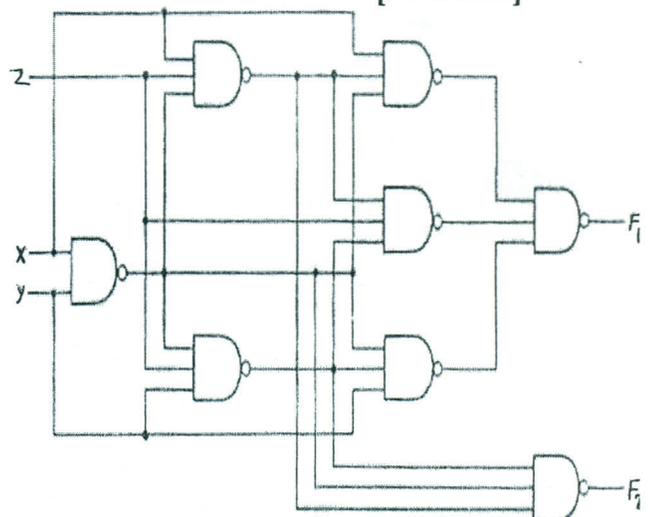

*with all best wishes*  
**Dr. Sabry F. Saraya**