



Answer the Following Five Questions:

Question (1) (20 Marks)

A series circuit consists of an A.C. supply 220V, 50 Hz, a switch, an inductor 0.2 H and a resistor 75 ohm. When the switch is closed at zero time, carry out the following;

- i) **derive** an expression for circuit current.
- ii) **determine**; (a) The extinction angle. (b) The average current. (c) The rms current.
(c) The power consumed by the load and input power factor.

Question (2) (20 Marks)

A single-phase fully-controlled thyristor converter feeding an RL load connected in series with a back emf E . Circuit data and load parameters are: $V = 220$ V, $f = 50$ Hz, $R = 1.5$ Ω , $L = 20$ mH and $E = 12$ V. For a trigger angle $\alpha = 60^\circ$, carry out the following;

- i) **Derive** an expression for the load current.
- ii) **Determine** (a) the average thyristor current. (b) the rms thyristor current.
(c) the rms output current. (d) the average load current.
(e) the critical delay angle α_c .

Question (3) (20 Marks)

A type A dc-chopper is feeding an RL load connected in series with a back emf E . Source voltage $V = 220$ V, chopping period $T = 2$ ms, on period = 1.0 ms, load circuit parameters: $R = 5$ Ω , $L = 15$ mH and $E = 12$ V.

- (a) Find whether load current is continuous or not.
- (b) Determine the value of average output current.
- (c) Determine the maximum and minimum values of steady state output current.
- (d) Sketch the time variations of gate signal i_g , load voltage v_o , load current i_o , thyristor current i_T freewheeling diode current i_{fd} and voltage across thyristor v_T .

Question (4) (20 Marks)


- (i) Derive expressions required to determine the filter parameters of an LC filter connected to the output terminals of a two-pulse single-phase rectifier feeding a resistive load.
- (ii) A single-phase two-pulse diode rectifier has input supply of 230 V, 50 Hz and a load resistance $R = 100$ Ω and load inductance $L_L = 10$ mH. An $L-C$ filter is to be used on the output side so as to reduce the output voltage ripple to 5%. Design the LC filter and determine the rms value of ripple voltage.

Question (5)

(20 Marks)

For the forced commutated thyristor circuit shown in the below figure:

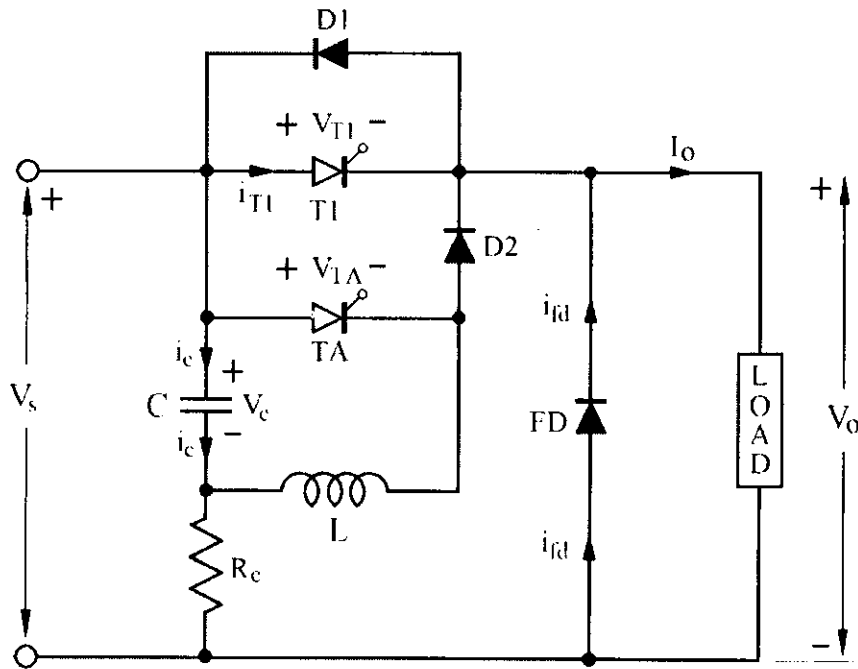- i) Derive mathematical expressions for the design of commutation parameters.
- ii) If the source voltage is 230 V dc and turn-off time of the main thyristor is 40 μ .sec. Determine the values of L and C for a load current of 500 A. Give any assumptions required for successful and safe operation. Also determine the peak values of capacitor voltage and commutation current.



End of Exam Questions – Good Luck