



Answer the following questions (The exam is two pages, two Smith charts and formula sheet): (Full Marks:70)

(Note: attach Smith charts with your booklet)

- 1.a) A microwave transistor has the following  $S$  parameters ( $Z_0 = 50 \Omega$ ):  $S_{11} = 0.8 \angle -90^\circ$ ,  
 $S_{21} = 5.1 \angle 80^\circ$ ,  $S_{12} = 0.3 \angle 70^\circ$ ,  $S_{22} = 0.62 \angle -40^\circ$ . Plot the stability circles of this transistor on the Smith chart and show the stable regions. Use horizontal lines ( $\equiv$ ) for shading the stable region of the input stability circle and vertical lines ( $\parallel$ ) for shading the stable region of the output stability circle. (7)
- b) In a designed microwave transistor amplifier for a specified gain the center and the radius of the constant gain input circle are given by:  $C_S = 0.706 \angle 120^\circ$ ,  $R_S = 0.166$ . The FET has the following scattering parameters ( $Z_0 = 50 \Omega$ ):  $S_{11} = 0.75 \angle -120^\circ$ ,  $S_{21} = 2.5 \angle 80^\circ$ ,  $S_{12} = 0.0$ ,  $S_{22} = 0.60 \angle -70^\circ$ . Calculate the gain of the input matching circuit in dB without using Smith chart. (6)
- c) A GaAs FET has the following the scattering and noise parameters at 8.0 GHz ( $Z_0 = 50 \Omega$ ):  
 $S_{11} = 0.7 \angle -110^\circ$ ,  $S_{21} = 3.5 \angle 60^\circ$ ,  $S_{12} = 0$ ,  $S_{22} = 0.8 \angle -70^\circ$ ,  $F_{\min} = 2.5 \text{ dB}$ ,  $\Gamma_{opt} = 0.70 \angle +120^\circ$ ,  
 $R_N = 15 \Omega$ . What are the values of  $\Gamma_S$  and  $\Gamma_L$  to obtain a low-noise amplifier with minimum noise figure, and maximum possible gain? Calculate the unilateral transducer power gain ( $G_{TU}$ ) in dB without using Smith chart. (7)
- 2.a) Sketch the circuit of a Colpitts oscillator using a common emitter transistor and derive the frequency of oscillation. (6)
- b) A one-port oscillator uses a negative-resistance diode having  $\Gamma_m = 2.05 \angle -60^\circ$  ( $Z_0 = 50 \Omega$ ) at its desired operating point, for  $f = 6 \text{ GHz}$ . Design the matching circuit for a load of  $50 \Omega$  using open-circuited shunt stub (take the upper intersecting point on the unity circle of the Smith chart). Sketch the circuit and show the lengths of the series and shunt sections. (7)
- c) Sketch the circuit diagram of a single-ended diode mixer and define the conversion loss. A down converter has a conversion loss of 4.17 dB and RF and LO isolation of 20 dB. If the RF input power is 0 dBm, what are the IF output power and the RF power leaked into the LO port? (7)
- 3.a) Sketch the schematic diagram of a two-cavity klystron and derive an expression for the bunching parameter ( $X$ ). Using this result find an expression for the optimum distance ( $L_{opt}$ ) between the two cavities. (7)
- b) A reflex klystron operates under the following conditions:  $V_o = 600 \text{ V}$ ,  $V_r = 250 \text{ V}$ ,  $f_r = 9 \text{ GHz}$ , and  $X'J_1(X') = 1.25$ .  $e/m = 1.76 \times 10^{11}$  (MKS system). Calculate the value of the repeller space for which the tube can oscillate in  $1^{3/4}$  mode ( $n=2$ ) and the electronic efficiency. (6)
- c) Show the state of the amplitude and the direction of propagation of each wave of the propagating waves in the TWT. A TWT operates under the following parameters:  $V_o = 3 \text{ kV}$ ,  $I_o = 30 \text{ mA}$ ,  $f = 10 \text{ GHz}$  and  $Z_o = 10 \Omega$ . If the interaction region is 16.24 cm long, find the power gain (in dBs) and the phase velocity of the forward growing wave. (7)

- 4.a) Sketch a top view of a circular magnetron oscillator. Find an expression for the cyclotron angular frequency. A circular magnetron has the following parameters:  $a = 2$  mm,  $b = 4$  mm,  $B_0 = 0.3$  Wb/m<sup>2</sup>, and  $N = 8$  cavities. Calculate the period for one complete revolution of the electron and the phase shift between two adjacent cavities for the 4<sup>th</sup> mode. (7)
- b) Write an expression for the capacitance of a varactor diode when a pumping voltage  $v_p = V_p \cos \omega_p t$  is applied on the diode. Sketch the equivalent circuit of a parametric amplifier. In an up-converter parametric amplifier; the figure of merit ( $\gamma Q$ ) is 10 and the ratio of the output frequency over the signal frequency ( $f_o / f_s$ ) is 20. Calculate the power gain. What is the power gain as predicted by Manley-Rowe (8)
-