



Please Answer The Followings:

1- For the circuit shown in Fig.1, find

(15 Mark)

- a-  $V_c(0^-)$ ,  $I(0^-)$ .
- b-  $V_c(t)$ ,  $I(t)$ .
- c- Energy stored in a capacitor and power dissipated in  $5\Omega$  resistance at  $t=2\tau$ .

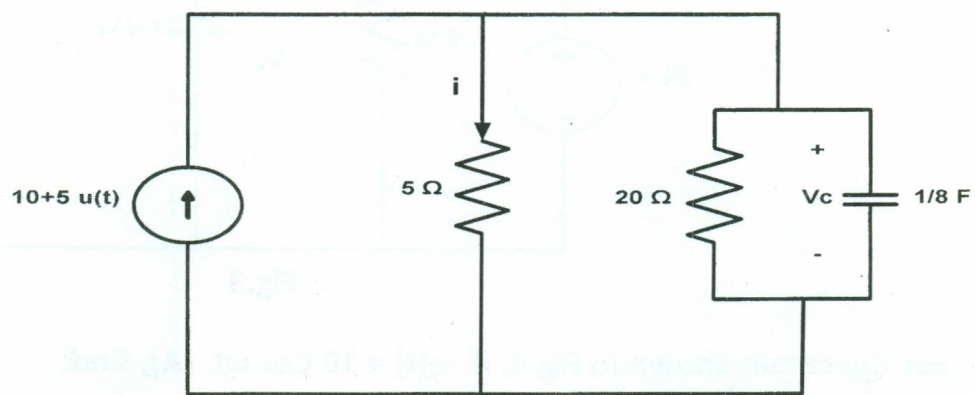


Fig. (1)

2- The linear transformer in the circuit shown in Fig.2 represents a two-port network. The voltage source  $V_s = 100$  V (r.m.s).

(30 Mark)

- a- Find the Z-parameters of the linear transformer.
- b- Under loading conditions of linear transformer, find  $I_1$ , total circuit impedance and power delivered by the source.
- c- Use the Z-parameters to derive the Thevenin's equivalent circuit with respect to  $R_L$  and find the maximum power absorbed by this resistance.

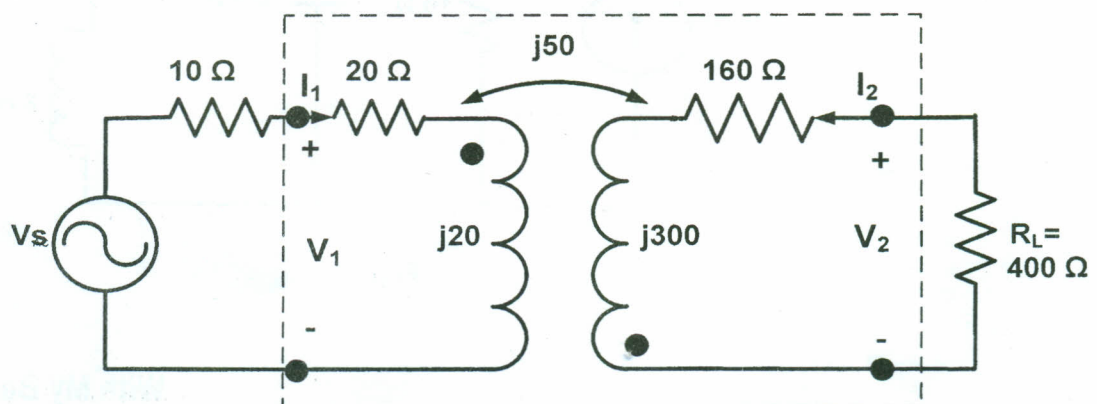


Fig.2

- 3- The switch in the circuit shown in Fig.3 has been open a long time before closing at  $t=0$ , find: (25 Mark)
- $i(0^+)$  and  $V_o(0^+)$ .
  - $i(t)$  for  $t \geq 0$ .
  - Energy stored in inductor at steady-state.

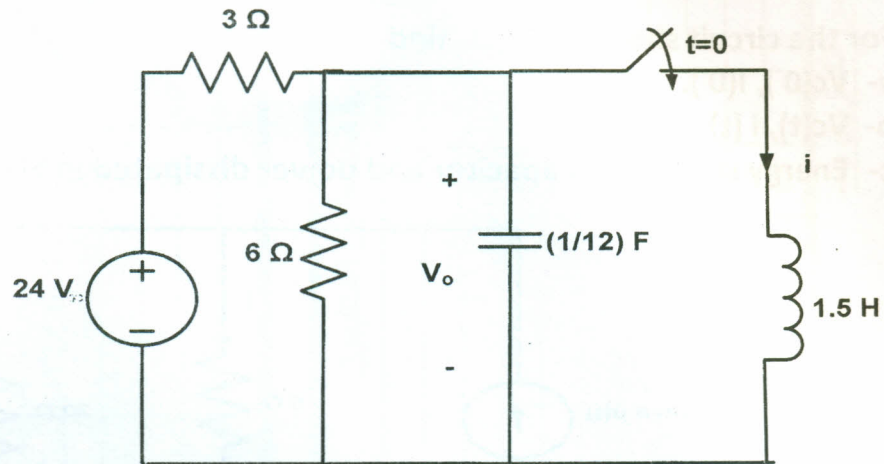


Fig.3

- 4- For the circuit shown in Fig.4, if  $I_s(t) = 10 \cos \omega t$  (A), find: (20Mark)
- Resonance frequency of the circuit ( $\omega_0$ ).
  - The magnitude of  $Y(\omega)$  at  $\omega=0$ ,  $\omega_0$ , and  $\infty$ .
  - Circuit quality factor (Q), bandwidth (B) and half power frequency points ( $\omega_1$ ,  $\omega_2$ ).
  - Power delivered by the current source at resonance and at  $\omega_1$ ,  $\omega_2$ .

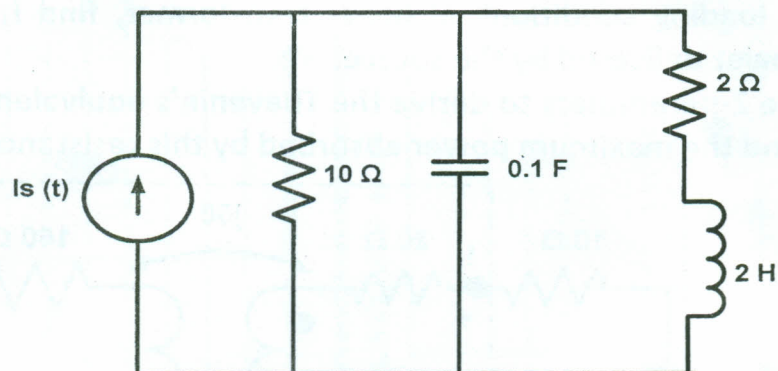


Fig.4

With My Best Wishes  
Prof. Dr. Mohammed El-Saied