

Mansoura University
 Faculty of Engineering
 Dept. of Electrical Eng.
**3rd year Electrical Engineering
 Students**
 Power electronics (1):
 [Dr. Khaled Abo-Al-Ez]



Second Semester
 2013/2014
 Time : (1:30) hr
 Full Mark : 45 Marks
 19/5/2014

Final Exam : Answer the following questions

Question (1):

- List the characteristics of an ideal power electronics switch.
- Derive the power losses in a transistor switch: Conduction losses, and Switching losses. Use needed diagrams and waveforms to support your answer.
- A transistor switch with the following characteristics controls power to a 25 kW load:

I_{RATED}	V_{RATED}	$I_{LEAKAGE}$	$V_{CE(SAT)}$	$t_{SW(ON)}$	$t_{SW(OFF)}$	Source voltage V_S	Load resistance R_L	Switching frequency f_s	Duty cycle (d)
50 A	500 V	1 mA	1.5 V	1.5 μ s	3 μ s	500 V	10 Ω	100 Hz	50%

Find:

- On-state and off-state power losses.
- Maximum power loss during turn-on.
- Energy losses during turn-on and turn-off.
- On-state and off-state energy losses.
- Total energy loss.
- Average power loss.

[15] Mark

Question (2):

- Sketch the schematic of a single phase full wave centre tapped transformer uncontrolled rectifier with a resistive (R) load, and an inductive (RL) load and explain the operation.
- A single phase full wave centre tapped transformer uncontrolled rectifier is supplied from a 50 V source. If the load resistance is 100 Ω . Find:
 - The average load voltage and the average load current.
 - The maximum value & the RMS value of the load current.
 - The peak inverse voltage (PIV) rating of a diode.
 - The rectifier efficiency.
 - Calculate the form factor, pulse number, ripple factor, conduction angle, and the power factor.

[15] Mark

Question (3):

- Sketch the schematic of a single phase half wave controlled rectifier with a resistive (R) load, and an inductive (RL) load and explain the operation.
- A single phase half wave controlled rectifier is supplied from a 120 V source. Calculate the firing angle necessary to deliver 150 W of power to a load resistance of 10 Ω .
- Sketch the schematic of a single phase full wave controlled bridge rectifier with a freewheeling diode that supplies an inductive (RL) load. If the supply voltage is 120 V and the resistive portion of the load is 10 Ω . Given that the delay angle is 30°. Find:
 - The average load voltage and the average load current.
 - The maximum value & the RMS value of the load current.
 - The average current in each SCR & the average current in the FWD.

[15] Mark

Dr. K. M. Abo-Al-Ez

Answer the following:

- 1- Sketch a collector steered base triggering circuit. Show the triggering waveforms, and explain the circuit functions. (10)
- 2- Sketch the logic symbol and the timing diagram for JK flip flop. Explain how JK flip flop differs from SC and D flip flops. (10)
- 3- Discuss the current and voltage requirements of a LED. Sketch the circuit symbol for the device and show how it employed in a seven segment numerical display.(10)
- 4- Sketch the whole circuits initiated from a counter of diode matrix for driving a seven segment display. Explain the operation of the circuit and identify the segment of the input display that are energized for each decimal.(15)