

Answer the following Questions:-

Q1- Find the critical clearing angle for the system shown in Fig.1 for a three phase fault at the point P. The generator is delivering 1.0 pu power under pre-fault conditions. ( 20 )

Q2- Synthesize the waveform of Fig.2 into its harmonic components. ( 18 )

Q3- A single-phase center tap controlled rectifier is operated with a firing angle  $\alpha$  of  $150^\circ$ . Provide plots for the load voltage, SCR<sub>1</sub> voltage and ac current assuming a continuous current case, i.e. large  $L_d$ . ( 25 )

Q4- Analyse the incident of capacitor switching depicted in fig.3. Calculate the characteristic impedance and the amplification factor. Also calculate them in the case of capacitor bank is 0.59; 175; 2.5 and 8.5 MVar. ( 25 )

Q5- A second-order damped filter is tuned to  $h_n \geq 17$ . Knowing  $X_c = 1.784 \Omega$  calculate the filter elements and plot its impedance. ( 22 )

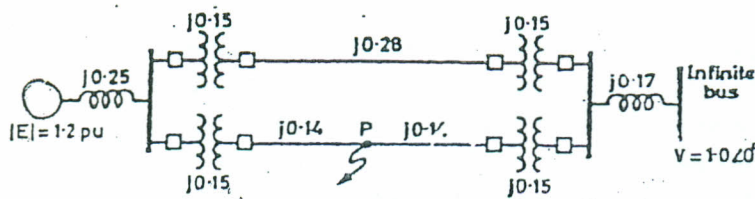


Fig. 1

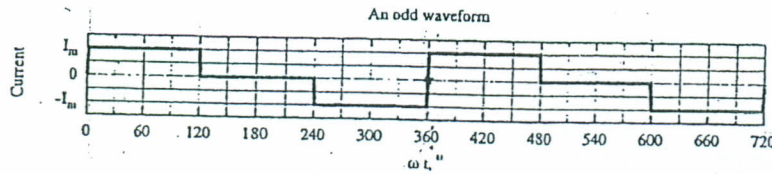


Fig. 2 A square waveform

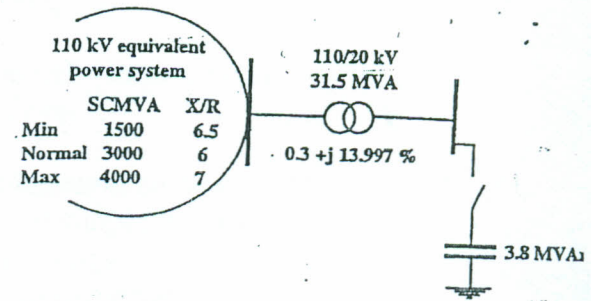


Fig. 3. Capacitor switching incident

مع أطيب دعواتي بالتوفيق والنجاح

Prof.Dr.Eng. I.I. Mansy