

Menofiya University
Faculty of Engineering
Dept of Mech. Power Engineering
Date: 1 /1/2014
Total Marks:90



Final Term Exam
Academic Year: 2013-2014
2nd Power
Allowed Time: 3 Hours

Subject/ Code: Measurements and Electronics / ELE217

This exam measures ILO's no. A3, B1, C1, C3, C4)

Remarks: No. of pages: 2 No. of questions: 6

Allowed Tables and Charts: (None)


Answer All The Following Questions:

The First Question (10- Marks)

- Define: Accuracy Sensitivity – Error-Types of Error
- A set of independent current measurements was taken by six observers and recorded as: 12.8 mA, 12.2 mA, 12.5 mA, 13.1 mA, 12.9 mA and 12.4 mA. Calculate:
 - The arithmetic mean
 - The deviations from the mean

The Second Question (20- Marks)

- Derive the torque equations of the PMMC instrument. Then, write the general equation of motion for the PMMC instrument.
- A basic d'Arsonval movement with internal resistance of 100Ω and half scale current deflection of 0.5 mA is to be converted into a multi-range d.c voltmeter with voltages ranges of 10V, 50V, 250V, and 500V. Calculate the value of the multiplier resistances for the multiple range dc voltmeter circuit shown.

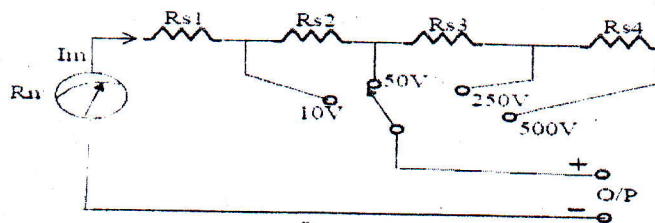

- A moving iron voltmeter reads correctly 250 Volt, when connected to 250 v (DC SUPPLY), determine its reading when connected to 250 v, 50 Hz (AC SUPPLY). The instrument coil has a resistance of 500Ω and an inductance of 1 H. (take the series non reactive resistance of 2000Ω)

The Third Question (15- Marks)

- Explain one kind of the wattmeter errors and how to Compensate it ?
- A 250 V -10 A dynamometer wattmeter has resistance for current and voltage coils of $0.5, 12500\Omega$ respectively. Find the percentage error when unity power factor load are connected at 250 volt for currents of 4 A.

Question (4)

[15]

- (a) Draw the block diagram of a basic oscilloscope. Describe briefly the function of each block. Then, show how it can be operated in the Y-t mode. If one cycle of 1.25 KHz sine wave fills exactly 8 divisions wide onto a CRT graticule, what is the setting of the Time/Div switch.
- (b) Draw and briefly explain, with the aid of timing diagram, the operation of a Mod-10 counter.
- (c) Using Linear Variable Differential Transformer (LVDT), show how to measure a liquid level in a tube.

Question (5)

[15]

- (a) In the common cathode 7-segment LED display, if the BCD number 0101 is applied to the BCD-to-7segment decoder/driver. What are the decoder/driver output and the decimal digit to be displayed.
- (b) Draw and explain the operation of a dual-slope digital voltmeter (DVM).
- (c) For a dual-slope DVM, derive expressions for the capacitor voltage during the charging and discharging periods. If $R = 10 \text{ K}\Omega$ and $C = 0.1 \mu\text{F}$ for the integrator. Also, if $V_X = 3 \text{ V}$ and $V_F = 5 \text{ V}$, calculate:
 - i) The integrator time constant.
 - ii) The capacitor charging and discharging currents.
 - iii) The charging and discharging slopes.

Question (6)

[15]

- (a) Using suitable transducer, show how to measure the strain on a metal bar. Avoid thermal effect.
- (b) A resistance strain gauge with a gauge factor of 4 is fastened to a steel bar that stretches from 25 to 25.01 cm. If the strained resistance value of the gauge is 125.2Ω , what is the resistance value before strain.
- (c) Using three decade counters with digital readout, show how to measure the frequency of a sinusoidal signal of about 6500 Hz. What is the time setting of COUNT in millisecond.

Good Luck